

Experiment 40

Friday, February 10, 2023 4:56 PM

Objectives:

1. Examine the specifications of an IC op amp.
2. Build and demonstrate the operation and characteristics of common op-amp circuits.

Lillian Tucker

Prelab-Information:

Inverting OpAmp

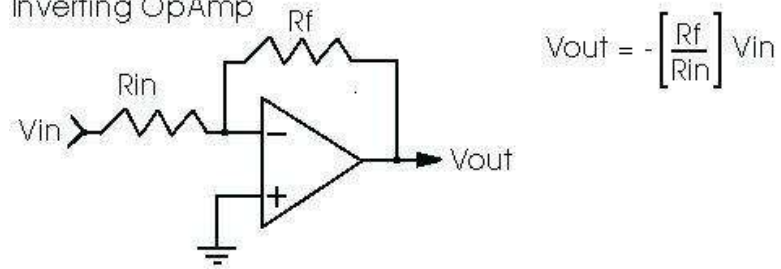


Figure 1 (Inverting Op Amp)

- $A = - \frac{R_f}{R_i} = \frac{V_{out}}{V_{in}}$
- $V_{out} = V_{in} \times A$

Procedure:

- Step 1-2:

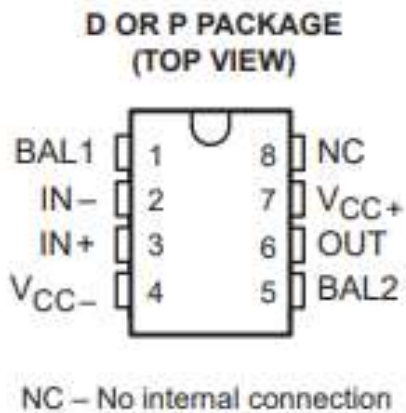


Figure 2 (LF411 Op Amp diagram)

Figure 3 (LF411 Info from Datasheet)

Max DC Supply [V]	Max Input [V]	Unity Gain [MHz]	Input Impedance [Ω]	Slew Rate [V/us]
18	15	3	10^{12}	13

- Step 4-5:

$$A = - \frac{R_f}{R_i} = \frac{V_{out}}{V_{in}}$$

$$V_{out} = V_{in} \times A$$

★ **NOTE:** Vin and Vout are not placed on proportionate graphs on oscilloscope. True values are annotated under each oscilloscope image

Experiment 40-2:

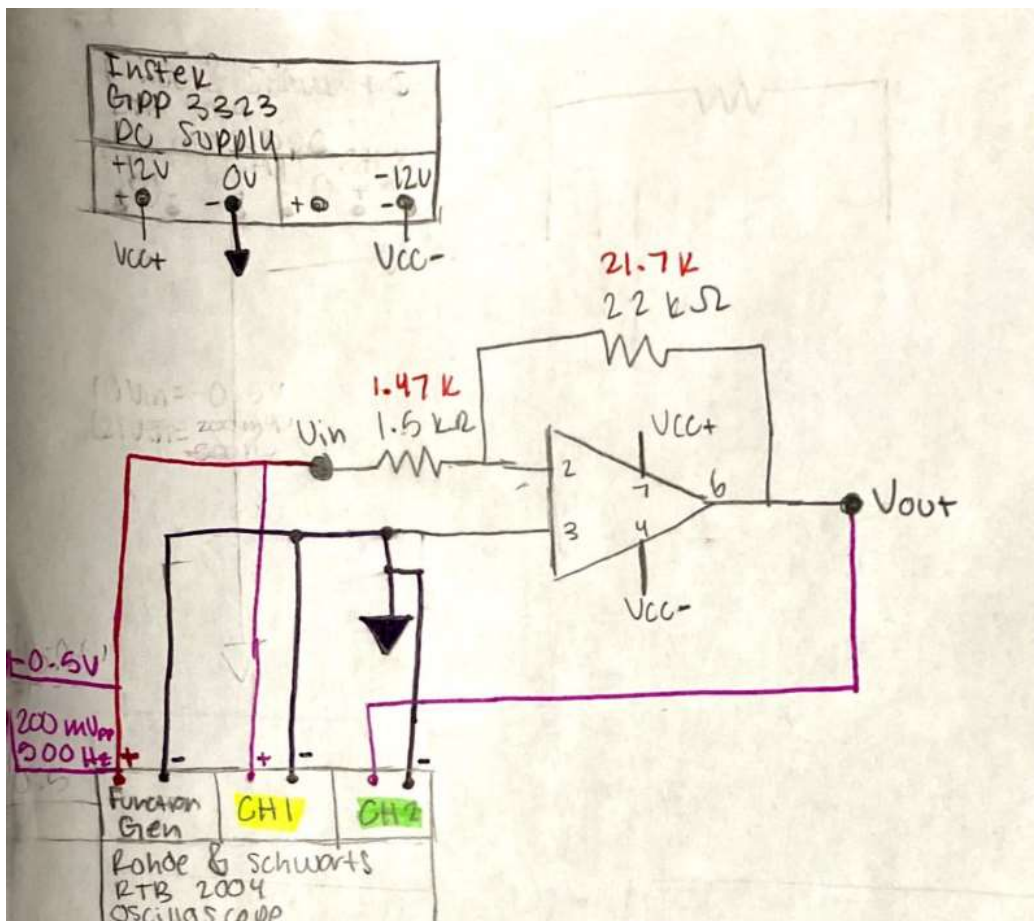


Figure 4 (Circuit Sketch with LF411, Power Supply, and Oscilloscope, Vin at pin 2)

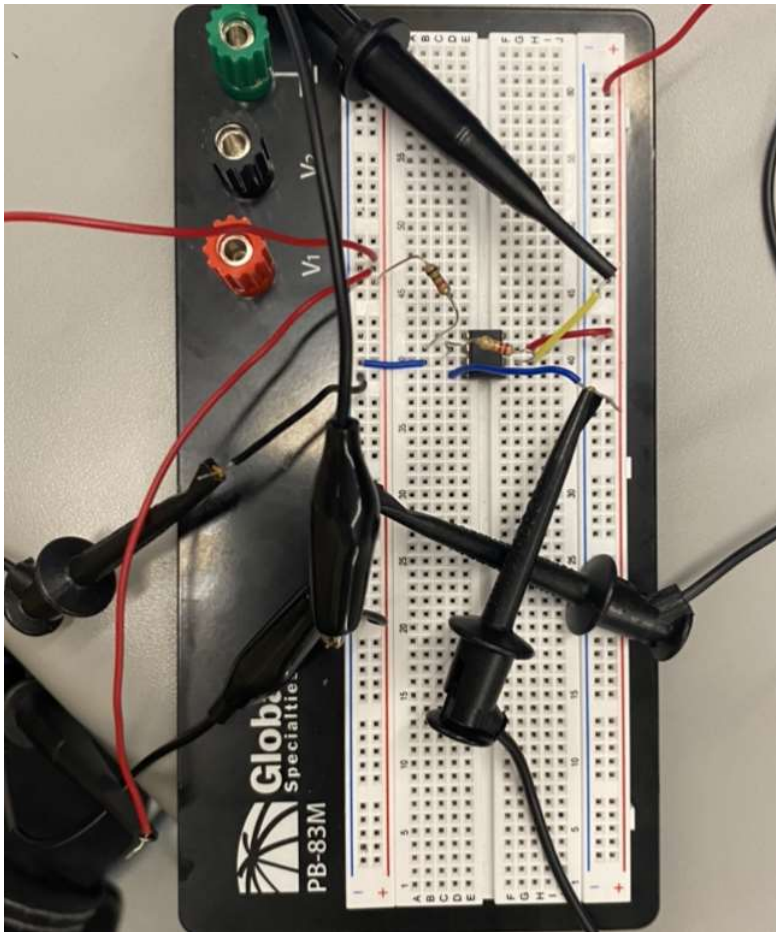


Figure 5 (Real Circuit Set Up: red = voltage sources, blue = -12 V, black = ground, yellow = oscilloscope channels)

Figure 6 (Calculated and measured circuit values)

DC	Input Voltage [V]	Output Voltage [V]	Output Saturation [V]	Gain
Calculated (Ideal)	-0.5	7.3	NA	-14.6
Calculated (Real)	-0.5	7.4	NA	-14.8
Measured	-0.5	7.1	NA	-14.2
AC/SINE	Input Voltage [mVpp]	Output Voltage [Vpp]	Output Saturation [Vpp]	Gain
Calculated (Ideal)	200	2.9	NA	-14.6
Calculated (Real)	200	3.0	NA	-14.8
Measured	200	3.0 < 90	11.5	15

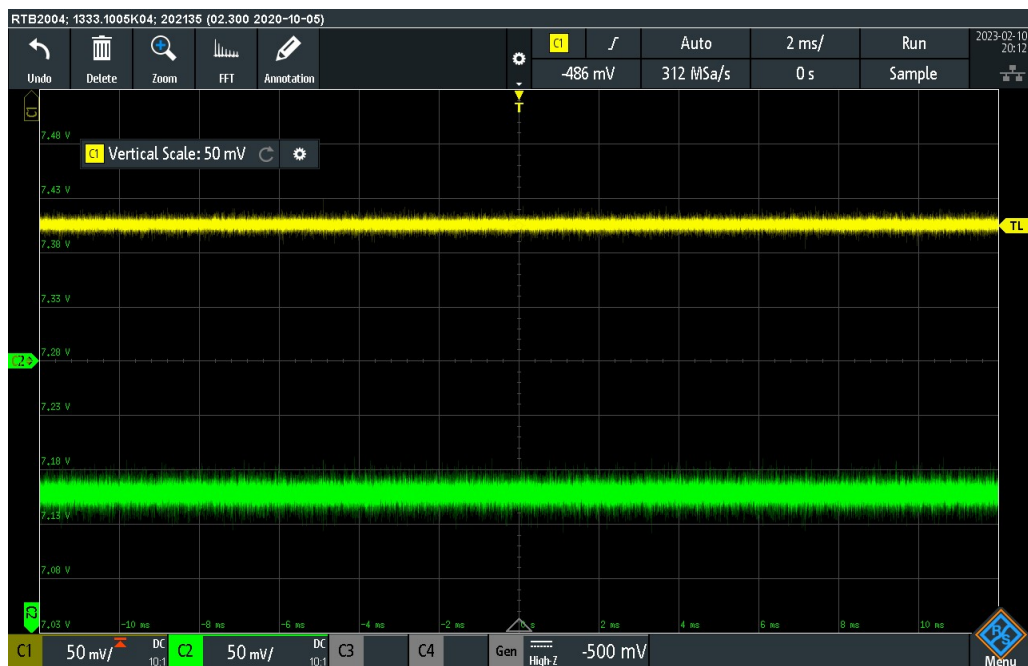


Figure 7 (Oscilloscope screenshot(DC Voltage): V_{in} (yellow channel 1) = -0.5 V, V_{out} (green channel 2) = 7.1 V)

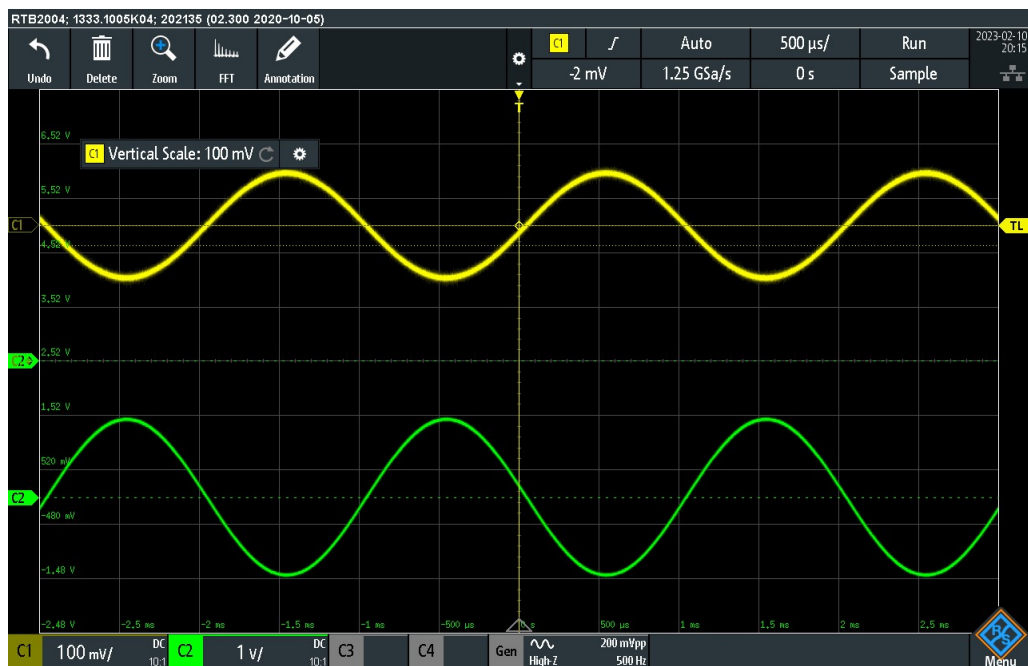


Figure 8 (Oscilloscope screenshot (AC/Sine Voltage): V_{in} (yellow channel 1) = 200 mVpp, V_{out} (green channel 2) = 1.5 Vpp)

Experiment 40-3:

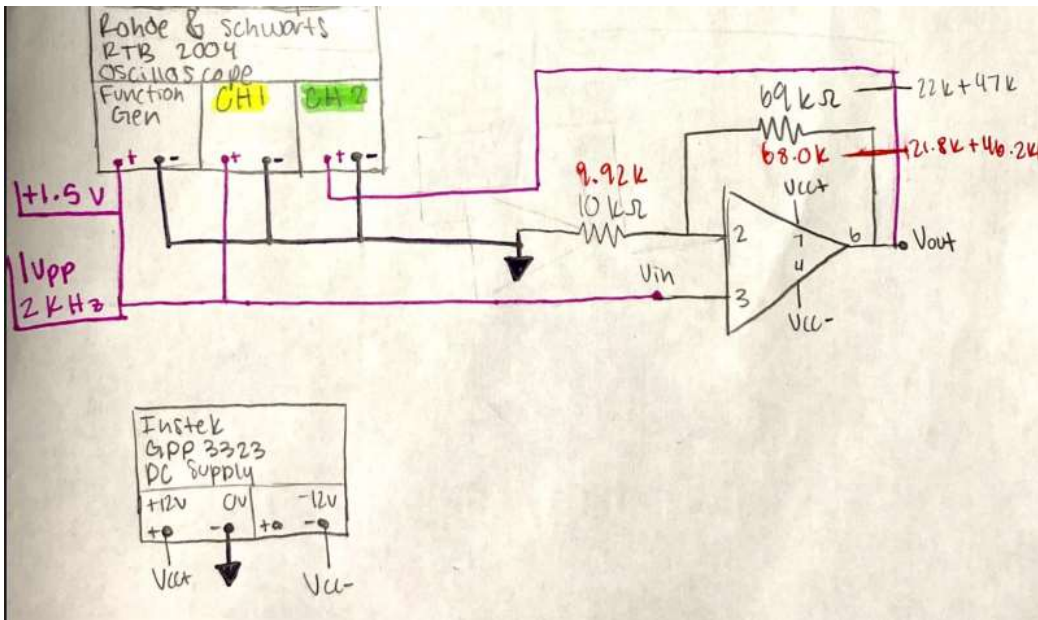


Figure 9(Circuit Sketch with LF411, Power Supply, and Oscilloscope, Vin at pin 3)

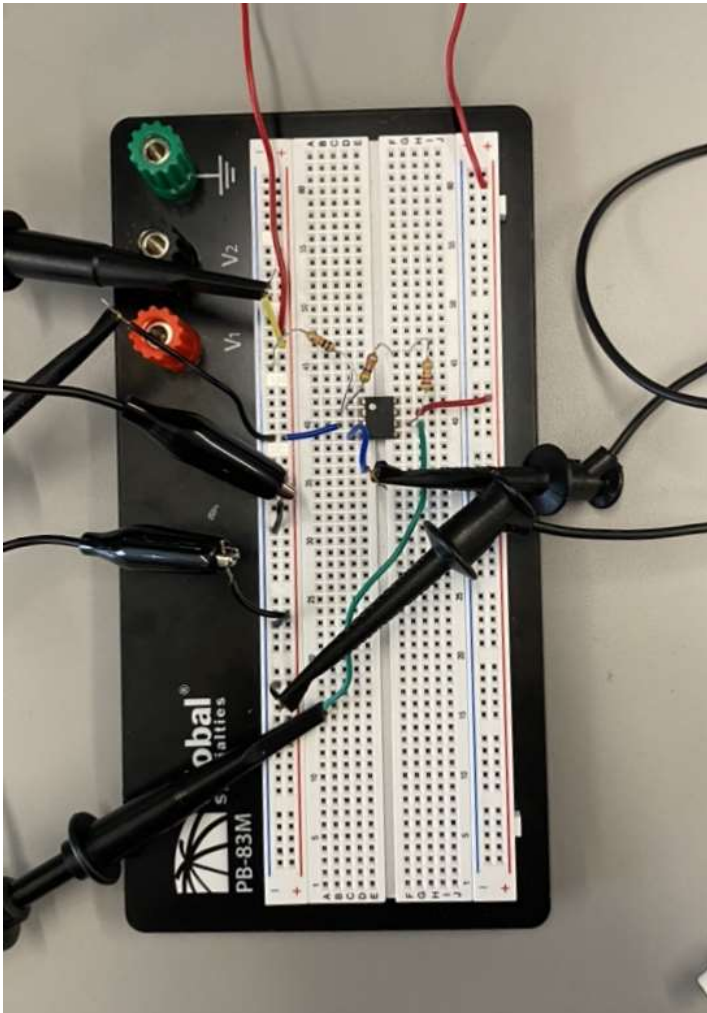


Figure 10 (Real Circuit Set Up: red = voltage sources, blue = -12 V, black = ground, yellow = channel 1, green = channel 2)

Figure 11 (Calculated and measured circuit values AC and DC)

DC	Input Voltage [V]	Output Voltage [V]	Output Saturation [V]	Gain
Calculated (Ideal)	+1.5	10.4	NA	-6.9
Calculated (Real)	+1.5	10.3	NA	-6.9

Measured	+1.5	11.3	NA	
AC/SINE	Input Voltage [mVpp]	Output Voltage [Vpp]	Output Saturation [Vpp]	Gain
Calculated (Ideal)	1	6.9	NA	-6.9
Calculated (Real)	1	6.9	NA	-6.9
Measured	1	5.5 < 0	11.5	5.5

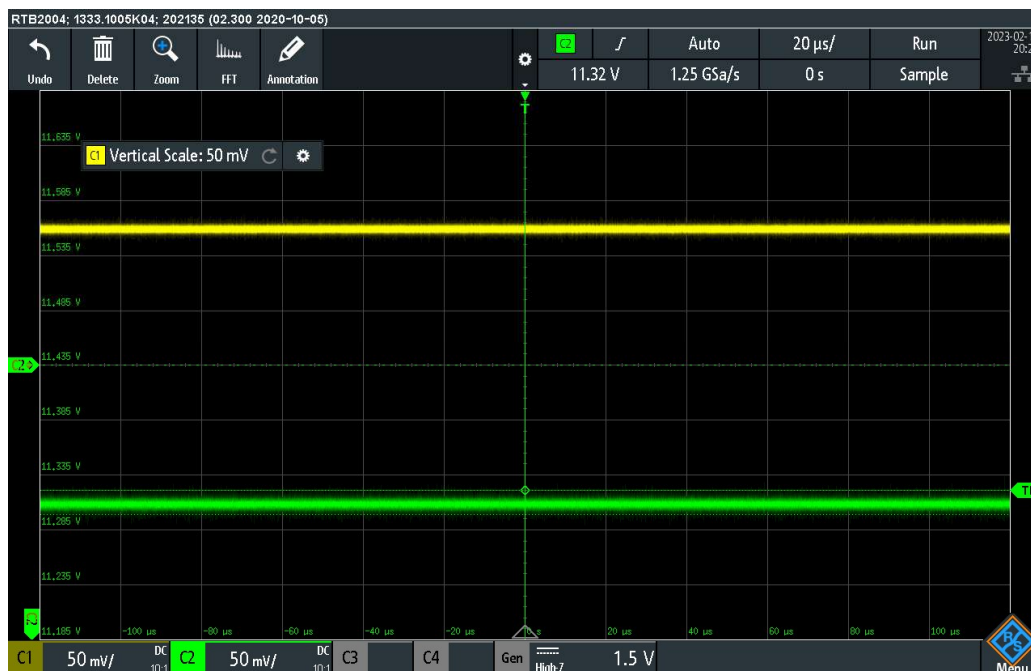


Figure 12 (Oscilloscope screenshot (DC Voltage): Vin (yellow channel 1) = +1.5 V, Vout (green channel 2) = 11.3 V

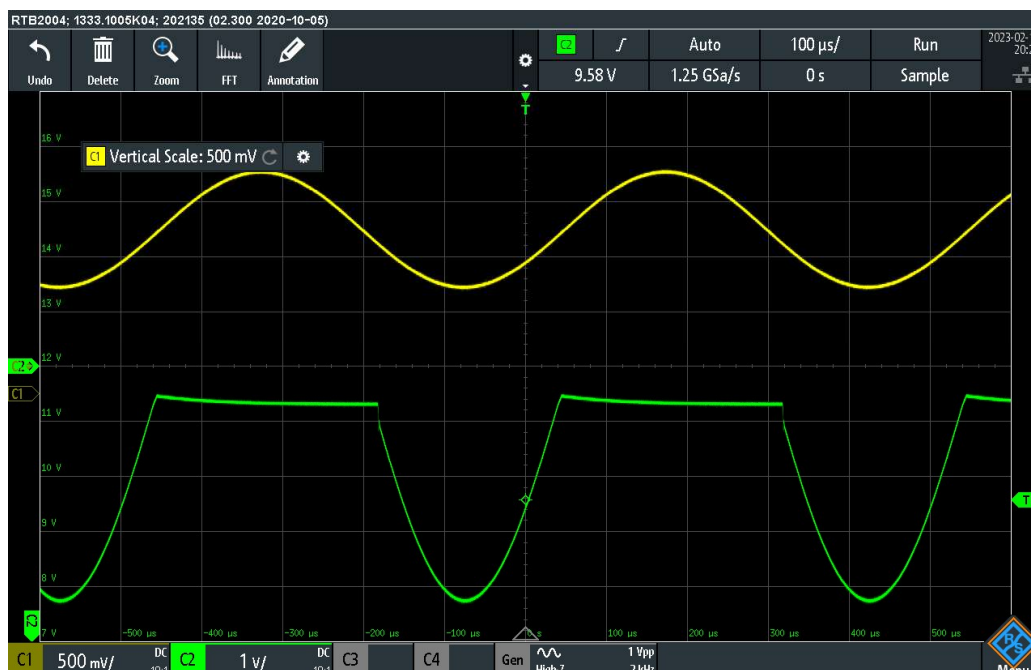


Figure 13 (Oscilloscope screenshot (AC/Sine Voltage): Vin (yellow channel 1) = 1 Vpp, Vout (green channel 2) = 5.5 Vpp - clipping/saturation at 11.5 Vpp
note for Figure 13: if voltage signal did not reach saturation, Vout \approx 6.9 Vpp so the Vout is more than half the predicted value)

Questions:

- Op amps amplify both dc and ac signals? a. True b. False
True
- An op-amp circuit could be made to have a gain of less than 1. a. True b. False
True
- What type of transistors are used to build this op amp. (See data sheet.)

