

1. Assume that you want to use a 10 kHz sinusoidal signal in the lab that has no DC component and swings from -1.0 V to +1.0 V. Fill in the blanks to refer to the 3 different ways you might refer to this signal. Show your work on the side for full credit. Assume no phase shift.

2 $V_{\text{peak-to-peak}}$ or V_{pp} $V_{pp} = 2 \cdot V_{pk} = 2 \cdot 1$

1 V_{peak} or V_{pk}

0.707 V_{RMS} $V_{RMS} = \frac{1}{\sqrt{2}} \cdot V_{pk} = \frac{1}{\sqrt{2}} \cdot 1$

2. How do the conversion formulas for V_{RMS} differ for V_{pk} and V_{pp} ? Write them below.

$$\begin{array}{l|l} V_{RMS} = \frac{1}{\sqrt{2}} \cdot V_{pk} & V_{pk} = \frac{1}{2} \cdot V_{pp} \\ V_{RMS} = \frac{1}{2\sqrt{2}} \cdot V_{pp} & V_{pp} = 2 \cdot V_{pk} \end{array}$$

(Figure 1: Question 1 & 2 solved)

3. Design a voltage divider using resistors and capacitors. Assume that V_{in} is your reference signal (show this on channel 1) and V_o is desired output signal (show this on channel 2). For this circuit assume that $\omega = 10000 \text{ rad/s}$ or 10 krad/s . A summary of design constraints:

- Resistors must be greater than 200Ω
- $|V_o| = 0.707 V_{in} = \frac{\sqrt{2}}{2} V_{in}$
- The phase of V_o must lead V_{in} by 45°

Draw and label your final design in the box. Also, state the frequency of V_{in} in Hz. Build and test this design.

Hint: what happens when $|X_c| = R$ in a voltage divider circuit?

(Figure 2: Question 3)

$$V_{in} = 4 V_{pp} = 2 V_p$$

$$V_o = \frac{\sqrt{2}}{2} \cdot V_{in} = 2.82842 V_{pp} = 1.41421 V_p$$

$$V_o = V_{in} \left(\frac{Z_2}{Z_1 + Z_2} \right)$$

$$1.414 \angle 45^\circ = 2 \left(\frac{Z_2}{Z_1 + Z_2} \right)$$

$$0.5 + j0.5 = \frac{Z_2}{Z_1 + Z_2}$$

$$Z_1 = (0.5 + j0.5) = Z_2 (0.5 + j0.5)$$



$$Z_1 = Z_2 \therefore \text{for a } 45^\circ \text{ phase shift, } R = C$$

$$R = 1000 \quad \omega = 10,000 \frac{\text{rad}}{\text{s}}$$


$$X_C = \frac{1}{j\omega C} \rightarrow -j1000 = \frac{1}{j(10,000)C}$$

$$\omega = \frac{10,000}{2\pi} = 1591.55 \text{ Hz}$$


$$C = 0.1 \mu\text{F}$$

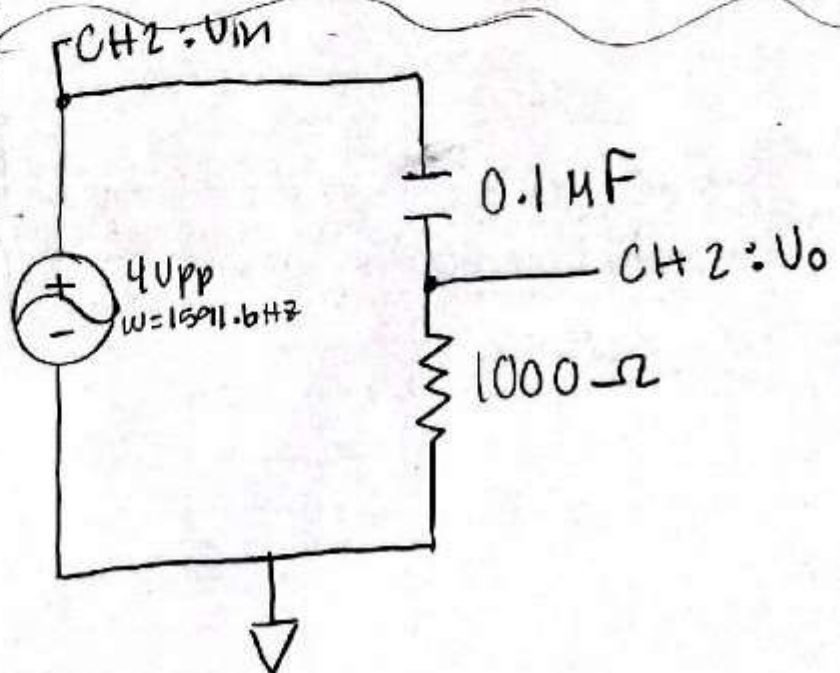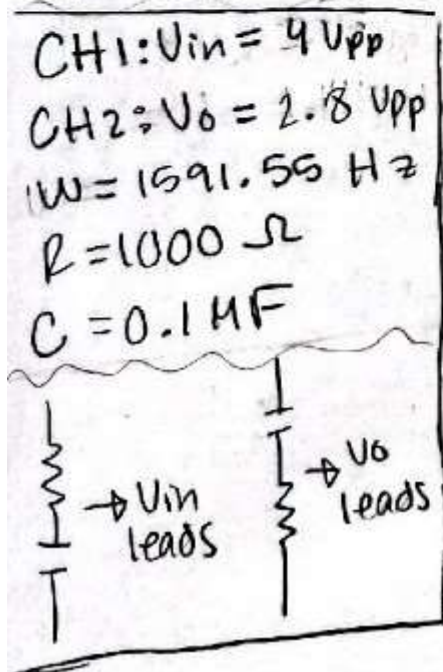

(Figure 3: Circuit Calculations and Design w Measurements)

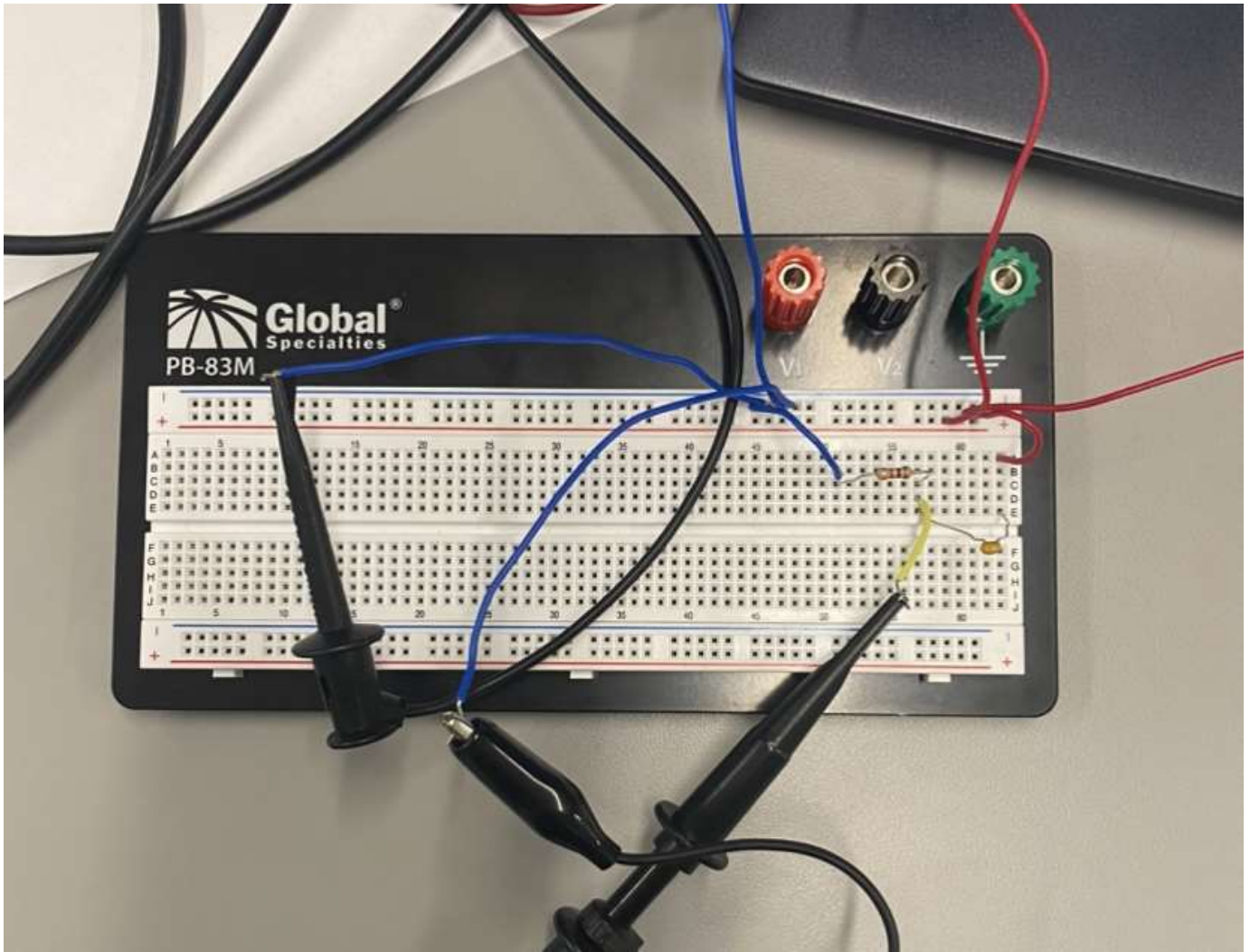

(Figure 4: Circuit Set Up)

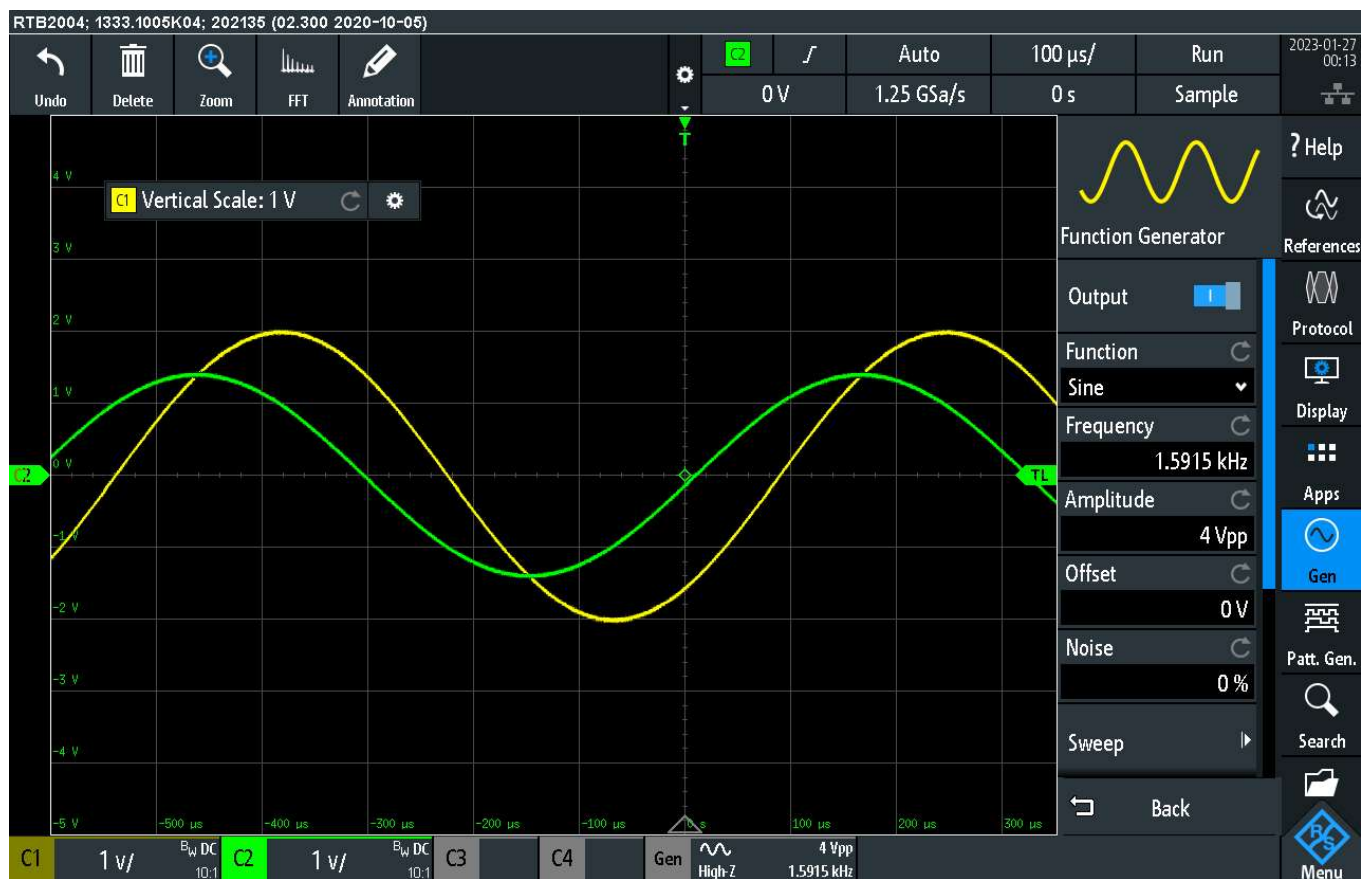

(Figure 5: Oscilloscope w Measurements and Function Generator)