

# Experiment 16

Sunday, January 29, 2023 3:32 PM

Lillian Tucker

## Objectives:


1. Demonstrate the storage capability of a capacitor.
2. Calculate and measure time constants in capacitor charge/discharge circuits.
3. Demonstrate the characteristics of a supercapacitor.

## Pre-Lab Information:

- CAPACITOR POLARITY MATTERS
- Steady State =  $5\tau$  (time constant)
- $\tau = RC$
- Charging Equation for voltage drop over C:  
$$v(t) = V_{ss}(1 - e^{-\frac{t}{\tau}})$$
 where  $\tau = RC$  and  $V_{ss}$  = steady state
- Discharging Equation for voltage drop over C:  
$$v(t) = V_0(e^{-\frac{t}{\tau}})$$
 where  $\tau = RC$  and  $V_0$  = initial voltage


## Procedure:

- Step 1-2:

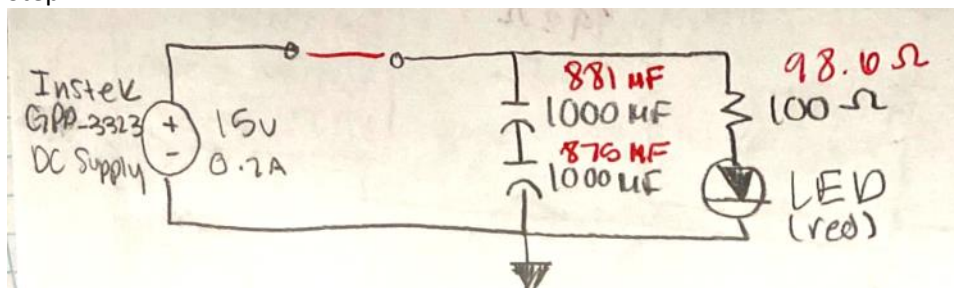

When the hookup wire is only connected to the capacitor, nothing happens. When the hookup wire is connected to both the capacitor and the LED/resistor, it lights to yellow for a fraction of a second then quickly turns on to a constant orange light. When the supply is turned off, the light fades to yellow (noticeably slower than when turned on) and then turns off

- Step 3-6:

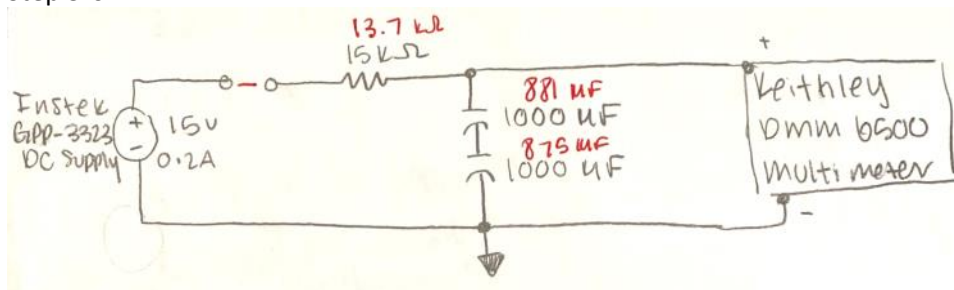

## Charging Capacitor:

$$v(t) = V_{ss}(1 - e^{-\frac{t}{\tau}})$$


$$v(\tau) = V_{ss}(1 - e^{-\frac{\tau}{\tau}})$$

$$v(\tau) = 15(1 - e^{-1})$$

$$v(\tau) = 9.48 V$$

$\tau$ [s] (theoretical)	$\tau$ [s] (real)	$5\tau$ [s] (real)
7.5 (ideal)	7.60	48.98
6.01 (actual)	7.55	44.33
	7.49	44.65

- Step 7:

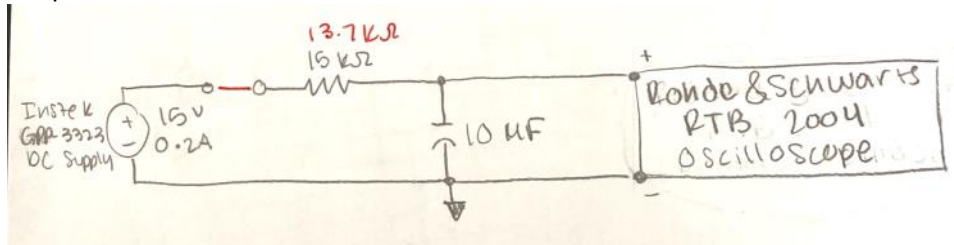

Charging Capacitor:

$$v(t) = V_{ss} \left(1 - e^{-\frac{t}{\tau}}\right)$$

$$v(\tau) = V_{ss} (1 - e^{-1})$$

$$v(\tau) = 15(1 - e^{-1})$$

$$v(\tau) = 9.48 \text{ V}$$


$\tau$ [ms] (theoretical)	$\tau$ [ms] (real)	$5\tau$ [ms] (real)
150 (ideal)	115 (LTSpice)	929 (LTSpice)
137 (actual)	210 (measured)	850 (measured)

Oscilloscope:




LTSpice Simulation:



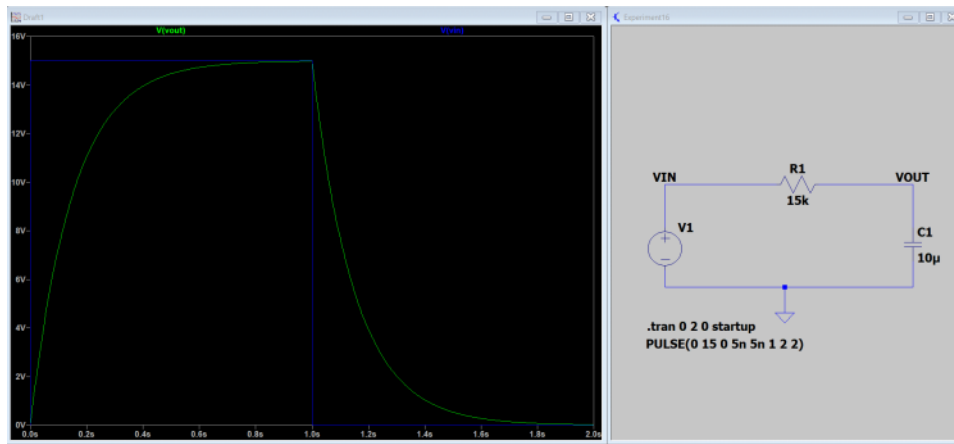

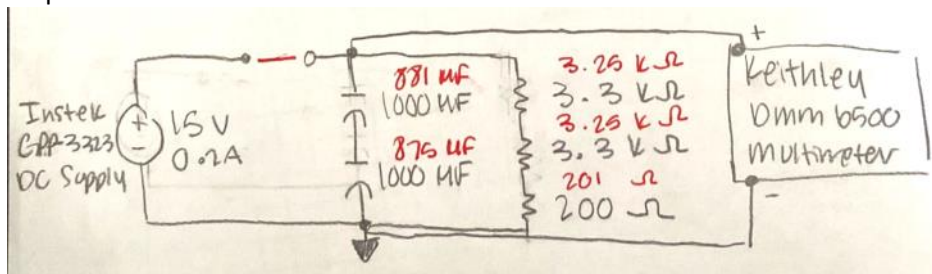- Step 8: A decrease in resistance would result in a smaller time constant, which means a shorter amount of time for the capacitor to charge and discharge.
- Step 9-11:



#### Discharging Capacitor:


$$v(t) = V_0 \left( e^{-\frac{t}{\tau}} \right)$$

$$v(\tau) = 15(e^{-1})$$

$$v(\tau) = 5.18 V$$

$\tau$ [s] (theoretical)	$\tau$ [s] (real)	$5\tau$ [s] (real)
3.4 (ideal)	4.08	25.87
2.94 (actual)	4.24	24.84
	4.15	24.71

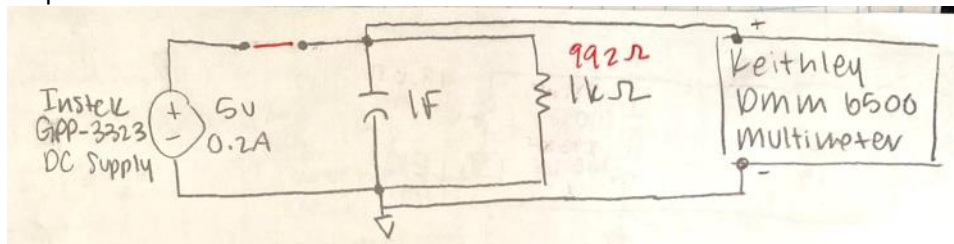- Step 12:  
An increase in capacitance would result in a larger time constant, which means a longer amount of time for the capacitor to charge and discharge.
- Step 13-15:



Charging Capacitor:

$$v(t) = V_{ss} \left(1 - e^{-\frac{t}{\tau}}\right)$$

$$v(\tau) = V_{ss} (1 - e^{-1})$$

$$v(\tau) = 5(1 - e^{-1})$$

$$v(\tau) = 3.16 \text{ V}$$

$\tau$ [s] (theoretical)	$\tau$ [s] (real)	$5\tau$ [s] (theoretical)
1000 (ideal)	1060.61	5303.05 (actual)
992 (actual)		5599.75 (measured)

Discharging Capacitor:

$$v(t) = V_0 \left(e^{-\frac{t}{\tau}}\right)$$

$$v(\tau) = 5(e^{-1})$$

$$v(\tau) = 1.16 \text{ V}$$

$\tau$ [s] (theoretical)	$\tau$ [s] (real)	$5\tau$ [s] (theoretical)
1000 (ideal)	1119.95	5303.05 (actual)
992 (actual)		5599.75 (measured)

**Questions:**

1. A supercapacitor makes a good replacement for a(n) \_\_\_\_\_ for some high-resistance, low-current circuits.

- Battery

2. What would be the capacitance and voltage rating of two 1-F, 5.5-V supercapacitors in series?

$$C_{eq} = \frac{C_1 * C_2}{C_1 + C_2} = \frac{1 * 1}{1 + 1}$$

$$C_{eq} = 0.5 \text{ F}$$

$$V_{eq} = V_1 + V_2 = 5.5 + 5.5$$

$$V_{eq} = 11 \text{ V}$$

3. Write the formulas for the charge and discharge curves of an RC circuit.

$$\text{Charge: } v(t) = V_{ss} \left(1 - e^{-\frac{t}{\tau}}\right) \text{ where } \tau = RC \text{ and } V_{ss} = \text{steady state}$$

$$\text{Discharge: } v(t) = V_0 \left(e^{-\frac{t}{\tau}}\right) \text{ where } \tau = RC \text{ and } V_0 = \text{initial voltage}$$